 


VHDL – TD2

1 Bascules

1.1 Bascule D avec remise à zéro asynchrone.

(DFF with asynchronous reset)



Avec un process ayant une liste de sensibilité.
(V.P 6-1)

```

1 -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY dff IS
6     PORT (d, clk, rst: IN STD_LOGIC;
7           q: OUT STD_LOGIC);
8 END dff;
9 -----
10 ARCHITECTURE behavior OF dff IS
11 BEGIN
12     PROCESS (clk, rst)
13     BEGIN
14         IF (rst='1') THEN
15             q <= '0';
16         ELSIF (clk'EVENT AND clk='1') THEN
17             q <= d;
18         END IF;
19     END PROCESS;
20 END behavior;
21 -----

```

Avec un process ayant un WAIT.
(V.P 6-4)

```

1 -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY dff IS
6     PORT (d, clk, rst: IN STD_LOGIC;
7           q: OUT STD_LOGIC);
8 END dff;

```

```

9 -----
10 ARCHITECTURE dff OF dff IS
11 BEGIN
12     PROCESS
13     BEGIN
14         WAIT ON rst, clk;
15         IF (rst='1') THEN
16             q <= '0';
17         ELSIF (clk'EVENT AND clk='1') THEN
18             q <= d;
19         END IF;
20     END PROCESS;
21 END dff;

```

Avec un process incluant un CASE.
(V.P 6-6)

```

1 -----
2 LIBRARY ieee;                                -- Unnecessary declaration,
3                                              -- because
4 USE ieee.std_logic_1164.all; -- BIT was used instead of
5                                              -- STD_LOGIC
6 -----
7 ENTITY dff IS
8     PORT (d, clk, rst: IN BIT;
9           q: OUT BIT);
10 END dff;
11 -----
12 ARCHITECTURE dff3 OF dff IS
13 BEGIN
14     PROCESS (clk, rst)
15     BEGIN
16         CASE rst IS
17             WHEN '1' => q<='0';
18             WHEN '0' =>
19                 IF (clk'EVENT AND clk='1') THEN
20                     q <= d;
21                 END IF;
22             WHEN OTHERS => NULL; -- Unnecessary, rst is of type
23                                   -- BIT
24         END CASE;
25     END PROCESS;
26 END dff3;

```

1.2 Bascule D avec sorties q et qbar .

(V.P 7-4)

Expliquer pourquoi la solution suivante est incorrecte. Proposer une solution correcte.

```

1 ---- Solution 1: not OK -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----

```

```

5 ENTITY dff IS
6   PORT ( d, clk: IN STD_LOGIC;
7         q: BUFFER STD_LOGIC;
8         qbar: OUT STD_LOGIC);
9 END dff;
10 -----
11 ARCHITECTURE not_ok OF dff IS
12 BEGIN
13   PROCESS (clk)
14   BEGIN
15     IF (clk'EVENT AND clk='1') THEN
16       q <= d;
17       qbar <= NOT q;
18     END IF;
19   END PROCESS;
20 END not_ok;
21 -----

```

Solution correcte (V.P 7-4)


```

1 ---- Solution 2: OK -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY dff IS
6   PORT ( d, clk: IN STD_LOGIC;
7         q: BUFFER STD_LOGIC;
8         qbar: OUT STD_LOGIC);
9 END dff;
10 -----
11 ARCHITECTURE ok OF dff IS
12 BEGIN
13   PROCESS (clk)
14   BEGIN
15     IF (clk'EVENT AND clk='1') THEN
16       q <= d;
17     END IF;
18   END PROCESS;
19   qbar <= NOT q; -- concurrent setting
20 END ok;
21 -----

```

 1.3 Latch

Le latch n'est pas une bascule, c'est une mémoire. Tant que clk est à '1', q prend les valeurs de d. Lorsque clk passe à '0', la dernière valeur de d est mémorisée. Programmer un Latch.




```

1 -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY latch IS
6     PORT (d, clk: IN STD_LOGIC;
7           q: OUT STD_LOGIC);
8 END latch;
9 -----
10 ARCHITECTURE behavior OF latch IS
11 BEGIN
12     PROCESS (clk, d)
13     BEGIN
14         IF (clk='1') THEN
15             q <= d;
16         END IF;
17     END PROCESS;
18 END behavior;
19 -----

```

2 Compteurs

2.1 Compteur décimal 1 chiffre

 

(V.P 6-2)

```

1 -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY counter IS
6     PORT (clk : IN STD_LOGIC;
7           digit : OUT INTEGER RANGE 0 TO 9);
8 END counter;
9 -----
10 ARCHITECTURE counter OF counter IS
11 BEGIN
12     count: PROCESS(clk)
13         VARIABLE temp : INTEGER RANGE 0 TO 10;
14     BEGIN
15         IF (clk'EVENT AND clk='1') THEN
16             temp := temp + 1;
17             IF (temp=10) THEN temp := 0;
18             END IF;
19         END IF;
20         digit <= temp;
21     END PROCESS count;
22 END counter;
23 -----

```

2.2 Compteur générique

On crée un paquetage “decimal” défini par:

```
PACKAGE decimal IS
  TYPE chiffre IS RANGE 0 TO 9;
  TYPE nombre IS ARRAY (INTEGER RANGE <>) OF chiffre;

  COMPONENT mod_cnt IS
    GENERIC(modulo: INTEGER:=16);
    PORT (clk, clear, cen: IN BIT;
          cout: OUT INTEGER RANGE 0 TO modulo-1;
          rco : OUT BIT);
  END COMPONENT mod_cnt;
END DECIMAL;
```

Le composant “mod_cnt” est un compteur modulo générique pour lequel on demande d’écrire la spécification en VHDL.

```
ENTITY mod_cnt IS
  GENERIC(modulo: INTEGER:=16);
  PORT (clk, clear, cen: IN BIT;
        cout: OUT INTEGER RANGE 0 TO modulo-1;
        rco : OUT BIT);
END mod_cnt;
```

```
-----
ARCHITECTURE cnt_beh OF mod_cnt IS
  SIGNAL state: INTEGER RANGE 0 TO modulo-1;
BEGIN
  rco <= cen WHEN state = modulo-1 ELSE '0';
  cout <= state;
  cnt: PROCESS
  BEGIN
    WAIT UNTIL clk = '1';
    IF clear = '1' THEN
      state <= 0;
    ELSIF cen = '1' THEN
      state <= (state + 1) mod modulo;
    END IF;
  END PROCESS cnt;
END cnt_beh;
```

Ce compteur est compilé dans une bibliothèque genlib. Expliquer comment l’instancier pour obtenir un compteur modulo 10 (entité decade).

```
USE work.decimal.all;

ENTITY decade IS
  PORT (clk, raz, en: IN BIT;
        cout: OUT chiffre;
        dix : OUT BIT);
END decade;

LIBRARY genlib ;
```

```

ARCHITECTURE instance OF decade IS
BEGIN
    dec : mod_cnt
        GENERIC MAP (modulo=>10)
        PORT MAP (clk=>clk, clear=>raz, cen=>en,
            cout=> integer(count), rco=>dix);
END instance;

```

```

-----
ARCHITECTURE cnt_beh OF mod_cnt IS
    SIGNAL state: INTEGER RANGE 0 TO modulo-1;
BEGIN
    rco <= cen WHEN state = modulo-1 ELSE '0';
    cout <= state;
    cnt: PROCESS
    BEGIN
        WAIT UNTIL clk = '1';
        IF clear = '1' THEN
            state <= 0;
        ELSIF cen = '1' THEN
            state <= (state + 1) mod modulo;
        END IF;
    END PROCESS cnt;
END cnt_beh;

```

3 Additionneurs

3.1 Additionneur avec propagation de retenue

(Carry Ripple Adder) La solution doit être élaborée à partir d'additionneurs complets 1 bit (1-bit full-adder). On demande une solution générique utilisant des STD_LOGIC_VECTORs et une solution non-générique utilisant les entiers.

(V.P 6-8)

```

1 ----- Solution 1: Generic, with VECTORS -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY adder IS
6     GENERIC (length : INTEGER := 8);
7     PORT ( a, b: IN STD_LOGIC_VECTOR (length-1 DOWNT0 0);
8           cin: IN STD_LOGIC;
9           s: OUT STD_LOGIC_VECTOR (length-1 DOWNT0 0);
10          cout: OUT STD_LOGIC);
11 END adder;
12 -----
13 ARCHITECTURE adder OF adder IS
14 BEGIN
15     PROCESS (a, b, cin)
16         VARIABLE carry : STD_LOGIC_VECTOR (length DOWNT0 0);

```

```

17 BEGIN
18     carry(0) := cin;
19     FOR i IN 0 TO length-1 LOOP
20         s(i) <= a(i) XOR b(i) XOR carry(i);
21         carry(i+1) := (a(i) AND b(i)) OR (a(i) AND
22             carry(i)) OR (b(i) AND carry(i));
23     END LOOP;
24     cout <= carry(length);
25 END PROCESS;
26 END adder;
27 -----


```

```

1 ---- Solution 2: non-generic, with INTEGERS ----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY adder IS
6     PORT ( a, b: IN INTEGER RANGE 0 TO 255;
7         c0: IN STD_LOGIC;
8         s: OUT INTEGER RANGE 0 TO 255;
9         c8: OUT STD_LOGIC);
10 END adder;
11 -----
12 ARCHITECTURE adder OF adder IS
13 BEGIN
14     PROCESS (a, b, c0)
15         VARIABLE temp: INTEGER RANGE 0 TO 511;
16     BEGIN
17         IF (c0='1') THEN temp:=1;
18         ELSE temp:=0;
19         END IF;
20         temp:= a + b + temp;
21         IF (temp > 255) THEN
22             c8 <= '1';
23             temp:= temp - 256;
24         ELSE c8 <= '0';
25         END IF;
26         s <= temp;
27     END PROCESS;
28 END adder;
29 -----

```

4 RAM

 

La mémoire a un bus d'entrée (data in), un bus d'adresse (addr), une horloge (clk) et une validation d'écriture (wr_en). Quand wr_en est activé, data in est rangé dans le mot d'adresse addr lors du front suivant de clk. Quant à la sortie data out elle doit en permanence afficher le mot sélectionné par addr. Le schéma de droite résume ce comportement.

Programmer une mémoire RAM générique de words mots de bits bits (défauts: bits=8 et words=16).

```

1 -----
2 LIBRARY ieee;
3 USE ieee.std_logic_1164.all;
4 -----
5 ENTITY ram IS
6     GENERIC ( bits: INTEGER:= 8; -- # of bits per word
7               words: INTEGER:= 16); -- # of words in the memory
8     PORT ( wr_ena, clk: IN STD_LOGIC;
9            addr: IN INTEGER RANGE 0 TO words-1;
10            data_in: IN STD_LOGIC_VECTOR (bits-1 DOWNT0 0);
11            data_out: OUT STD_LOGIC_VECTOR (bits-1 DOWNT0 0));
12 END ram;
13 -----
14 ARCHITECTURE ram OF ram IS
15     TYPE vector_array IS ARRAY (0 TO words-1) OF
16         STD_LOGIC_VECTOR (bits-1 DOWNT0 0);
17     SIGNAL memory: vector_array;
18 BEGIN
19     PROCESS (clk, wr_ena)
20     BEGIN
21         IF (wr_ena='1') THEN
22             IF (clk'EVENT AND clk='1') THEN
23                 memory(addr) <= data_in;
24             END IF;
25         END IF;
26     END PROCESS;
27     data_out <= memory(addr);
28 END ram;
29 -----

```

Cette RAM générique est compilée dans la bibliothèque mem. Expliquer comment instancier une RAM de 16 mots de 8 bits.

```

USE work.mem.all;

ENTITY ram16x8 IS
    PORT ( wr_ena, clk: IN STD_LOGIC;
           addr: IN INTEGER RANGE 0 TO words-1;
           data_in: IN STD_LOGIC_VECTOR (bits-1 DOWNT0 0);
           data_out: OUT STD_LOGIC_VECTOR (bits-1 DOWNT0 0));
    END ram;
-----

ARCHITECTURE ram16x8 OF ram IS
BEGIN
    Inst: ram
        GENERIC MAP (
            words => 16,
            bits => 8
        )
        PORT MAP (
            addr => addrBus,
            data_in => dataBus1,
            wr_en => w,
            clk => h,
            data_out => dataBus2
        );
END ram16x8;

```